

Exercise 13

A series circuit consists of a resistor with $R = 20 \Omega$, an inductor with $L = 1 \text{ H}$, a capacitor with $C = 0.002 \text{ F}$, and a 12-V battery. If the initial charge and current are both 0, find the charge and current at time t .

Solution

The equation for the charge in a circuit consisting of an inductor, a resistor, and a capacitor in series with a battery is given by

$$L \frac{d^2 Q}{dt^2} + R \frac{dQ}{dt} + \frac{1}{C} Q = V.$$

Since there's zero charge and no current initially, the initial conditions associated with this ODE are $Q(0) = 0$ and $Q'(0) = 0$. Because the ODE is linear, the general solution can be written as the sum of a complementary solution and a particular solution.

$$Q = Q_c + Q_p$$

The complementary solution satisfies the associated homogeneous equation.

$$L \frac{d^2 Q_c}{dt^2} + R \frac{dQ_c}{dt} + \frac{1}{C} Q_c = 0. \quad (1)$$

Because this ODE is homogeneous and has constant coefficients, it has solutions of the form $Q_c = e^{rt}$.

$$Q_c = e^{rt} \quad \rightarrow \quad \frac{dQ_c}{dt} = r e^{rt} \quad \rightarrow \quad \frac{d^2 Q_c}{dt^2} = r^2 e^{rt}$$

Substitute these formulas into equation (1).

$$L(r^2 e^{rt}) + R(r e^{rt}) + \frac{1}{C}(e^{rt}) = 0$$

Divide both sides by e^{rt} .

$$Lr^2 + Rr + \frac{1}{C} = 0$$

Multiply both sides by C .

$$LCr^2 + RCr + 1 = 0$$

Solve for r , noting that $R^2 C^2 - 4LC < 0$.

$$r = \frac{-RC \pm i\sqrt{4LC - R^2 C^2}}{2LC}$$

$$r = \left\{ \frac{-RC - i\sqrt{4LC - R^2 C^2}}{2LC}, \frac{-RC + i\sqrt{4LC - R^2 C^2}}{2LC} \right\}$$

Two solutions to the ODE are

$$\exp\left(\frac{-RC - i\sqrt{4LC - R^2 C^2}}{2LC} t\right) \quad \text{and} \quad \exp\left(\frac{-RC + i\sqrt{4LC - R^2 C^2}}{2LC} t\right).$$

According to the principle of superposition, the general solution to equation (1) is a linear combination of these two.

$$\begin{aligned}
 Q_c(t) &= C_1 \exp\left(\frac{-RC - i\sqrt{4LC - R^2C^2}}{2LC}t\right) + C_2 \exp\left(\frac{-RC + i\sqrt{4LC - R^2C^2}}{2LC}t\right) \\
 &= C_1 \exp\left(-\frac{R}{2L}t\right) \exp\left(-i\frac{\sqrt{4LC - R^2C^2}}{2LC}t\right) + C_2 \exp\left(-\frac{R}{2L}t\right) \exp\left(i\frac{\sqrt{4LC - R^2C^2}}{2LC}t\right) \\
 &= \exp\left(-\frac{R}{2L}t\right) \left[C_1 \exp\left(-i\frac{\sqrt{4LC - R^2C^2}}{2LC}t\right) + C_2 \exp\left(i\frac{\sqrt{4LC - R^2C^2}}{2LC}t\right) \right] \\
 &= \exp\left(-\frac{R}{2L}t\right) \left[C_1 \left(\cos\frac{\sqrt{4LC - R^2C^2}}{2LC}t - i \sin\frac{\sqrt{4LC - R^2C^2}}{2LC}t \right) \right. \\
 &\quad \left. + C_2 \left(\cos\frac{\sqrt{4LC - R^2C^2}}{2LC}t + i \sin\frac{\sqrt{4LC - R^2C^2}}{2LC}t \right) \right] \\
 &= \exp\left(-\frac{R}{2L}t\right) \left[(C_1 + C_2) \cos\frac{\sqrt{4LC - R^2C^2}}{2LC}t + (-iC_1 + iC_2) \sin\frac{\sqrt{4LC - R^2C^2}}{2LC}t \right] \\
 &= \exp\left(-\frac{R}{2L}t\right) \left(C_3 \cos\frac{\sqrt{4LC - R^2C^2}}{2LC}t + C_4 \sin\frac{\sqrt{4LC - R^2C^2}}{2LC}t \right)
 \end{aligned}$$

On the other hand, the particular solution satisfies the original ODE.

$$L \frac{d^2 Q_p}{dt^2} + R \frac{dQ_p}{dt} + \frac{1}{C} Q_p = V \quad (2)$$

The inhomogeneous term is a polynomial of degree 0, so the trial solution is $Q_p = A$.

$$Q_p = A \quad \rightarrow \quad \frac{dQ_p}{dt} = 0 \quad \rightarrow \quad \frac{d^2 Q_p}{dt^2} = 0$$

Substitute these formulas into equation (2).

$$L(0) + R(0) + \frac{1}{C}(A) = V$$

Solve for A .

$$A = CV$$

The particular solution is then

$$Q_p = CV,$$

and the general solution to the original ODE is

$$\begin{aligned}
 Q(t) &= Q_c + Q_p \\
 &= \exp\left(-\frac{R}{2L}t\right) \left(C_3 \cos\frac{\sqrt{4LC - R^2C^2}}{2LC}t + C_4 \sin\frac{\sqrt{4LC - R^2C^2}}{2LC}t \right) + CV.
 \end{aligned}$$

Differentiate it with respect to t .

$$\begin{aligned} \frac{dQ}{dt} = & -\frac{R}{2L} \exp\left(-\frac{R}{2L}t\right) \left(C_3 \cos \frac{\sqrt{4LC - R^2C^2}}{2LC}t + C_4 \sin \frac{\sqrt{4LC - R^2C^2}}{2LC}t \right) \\ & + \exp\left(-\frac{R}{2L}t\right) \left(-C_3 \frac{\sqrt{4LC - R^2C^2}}{2LC} \sin \frac{\sqrt{4LC - R^2C^2}}{2LC}t \right. \\ & \left. + C_4 \frac{\sqrt{4LC - R^2C^2}}{2LC} \cos \frac{\sqrt{4LC - R^2C^2}}{2LC}t \right) \end{aligned}$$

Apply the initial conditions to determine C_3 and C_4 .

$$Q(0) = C_3 + CV = 0$$

$$\frac{dQ}{dt}(0) = -\frac{R}{2L}C_3 + C_4 \frac{\sqrt{4LC - R^2C^2}}{2LC} = 0$$

Solving this system yields

$$C_3 = -CV \quad \text{and} \quad C_4 = -\frac{RVC^2}{\sqrt{4LC - R^2C^2}}.$$

Therefore,

$$Q(t) = \exp\left(-\frac{R}{2L}t\right) \left(-CV \cos \frac{\sqrt{4LC - R^2C^2}}{2LC}t - \frac{RVC^2}{\sqrt{4LC - R^2C^2}} \sin \frac{\sqrt{4LC - R^2C^2}}{2LC}t \right) + CV.$$


Plug in $R = 20 \, \Omega$, $L = 1 \, \text{H}$, $C = 0.002 \, \text{F}$, and $V = 12 \, \text{V}$.

$$Q(t) = e^{-10t}(-0.024 \cos 20t - 0.012 \sin 20t) + 0.024$$

Differentiate this with respect to t to get the current.

$$\begin{aligned} I(t) = \frac{dQ}{dt} &= -10e^{-10t}(-0.024 \cos 20t - 0.012 \sin 20t) + e^{-10t}(0.48 \sin 20t - 0.24 \cos 20t) \\ &= 0.6e^{-10t} \sin 20t \end{aligned}$$

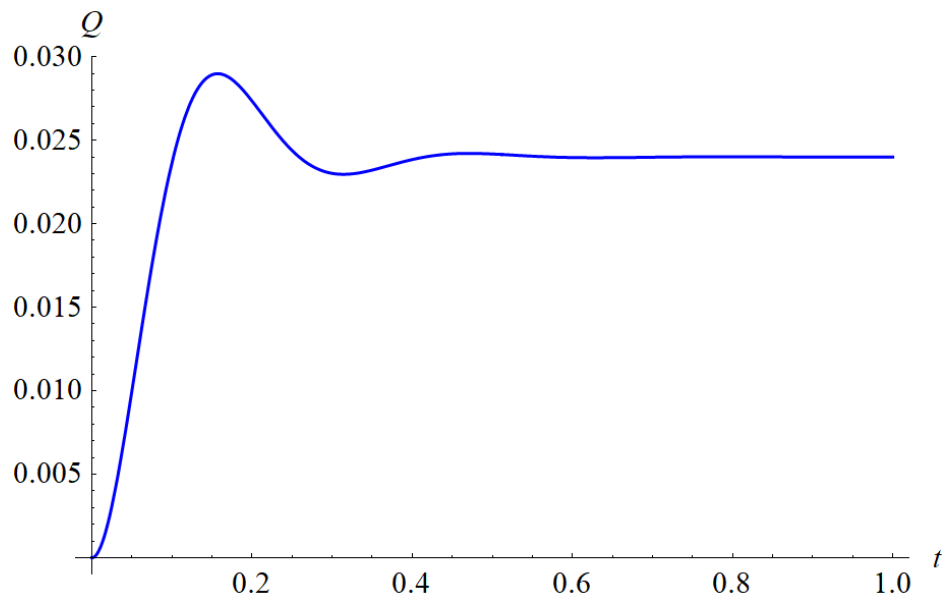Below is a plot of the charge versus time.



Below is a plot of the current versus time.

