

Exercise 16

The battery in Exercise 14 is replaced by a generator producing a voltage of $E(t) = 12 \sin 10t$.

- Find the charge at time t .
- Graph the charge function.

Solution

The equation for the charge in a circuit consisting of an inductor, a resistor, and a capacitor in series with this generator is given by

$$L \frac{d^2 Q}{dt^2} + R \frac{dQ}{dt} + \frac{1}{C} Q = 12 \sin 10t.$$

Since there's zero charge and no current initially, the initial conditions associated with this ODE are $Q(0) = 0.001$ and $Q'(0) = 0$. Because the ODE is linear, the general solution can be written as the sum of a complementary solution and a particular solution.

$$Q = Q_c + Q_p$$

The complementary solution satisfies the associated homogeneous equation.

$$L \frac{d^2 Q_c}{dt^2} + R \frac{dQ_c}{dt} + \frac{1}{C} Q_c = 0. \quad (1)$$

Because this ODE is homogeneous and has constant coefficients, it has solutions of the form $Q_c = e^{rt}$.

$$Q_c = e^{rt} \quad \rightarrow \quad \frac{dQ_c}{dt} = r e^{rt} \quad \rightarrow \quad \frac{d^2 Q_c}{dt^2} = r^2 e^{rt}$$

Substitute these formulas into equation (1).

$$L(r^2 e^{rt}) + R(r e^{rt}) + \frac{1}{C}(e^{rt}) = 0$$

Divide both sides by e^{rt} .

$$Lr^2 + Rr + \frac{1}{C} = 0$$

Multiply both sides by C .

$$LCr^2 + RCr + 1 = 0$$

Solve for r , noting that $R^2 C^2 - 4LC < 0$.

$$r = \frac{-RC \pm i\sqrt{4LC - R^2 C^2}}{2LC}$$

$$r = \left\{ \frac{-RC - i\sqrt{4LC - R^2 C^2}}{2LC}, \frac{-RC + i\sqrt{4LC - R^2 C^2}}{2LC} \right\}$$

Two solutions to the ODE are

$$\exp\left(\frac{-RC - i\sqrt{4LC - R^2 C^2}}{2LC} t\right) \quad \text{and} \quad \exp\left(\frac{-RC + i\sqrt{4LC - R^2 C^2}}{2LC} t\right).$$

According to the principle of superposition, the general solution to equation (1) is a linear combination of these two.

$$\begin{aligned}
 Q_c(t) &= C_1 \exp\left(\frac{-RC - i\sqrt{4LC - R^2C^2}}{2LC}t\right) + C_2 \exp\left(\frac{-RC + i\sqrt{4LC - R^2C^2}}{2LC}t\right) \\
 &= C_1 \exp\left(-\frac{R}{2L}t\right) \exp\left(-i\frac{\sqrt{4LC - R^2C^2}}{2LC}t\right) + C_2 \exp\left(-\frac{R}{2L}t\right) \exp\left(i\frac{\sqrt{4LC - R^2C^2}}{2LC}t\right) \\
 &= \exp\left(-\frac{R}{2L}t\right) \left[C_1 \exp\left(-i\frac{\sqrt{4LC - R^2C^2}}{2LC}t\right) + C_2 \exp\left(i\frac{\sqrt{4LC - R^2C^2}}{2LC}t\right) \right] \\
 &= \exp\left(-\frac{R}{2L}t\right) \left[C_1 \left(\cos\frac{\sqrt{4LC - R^2C^2}}{2LC}t - i \sin\frac{\sqrt{4LC - R^2C^2}}{2LC}t \right) \right. \\
 &\quad \left. + C_2 \left(\cos\frac{\sqrt{4LC - R^2C^2}}{2LC}t + i \sin\frac{\sqrt{4LC - R^2C^2}}{2LC}t \right) \right] \\
 &= \exp\left(-\frac{R}{2L}t\right) \left[(C_1 + C_2) \cos\frac{\sqrt{4LC - R^2C^2}}{2LC}t + (-iC_1 + iC_2) \sin\frac{\sqrt{4LC - R^2C^2}}{2LC}t \right] \\
 &= \exp\left(-\frac{R}{2L}t\right) \left(C_3 \cos\frac{\sqrt{4LC - R^2C^2}}{2LC}t + C_4 \sin\frac{\sqrt{4LC - R^2C^2}}{2LC}t \right)
 \end{aligned}$$

On the other hand, the particular solution satisfies the original ODE.

$$L \frac{d^2 Q_p}{dt^2} + R \frac{dQ_p}{dt} + \frac{1}{C} Q_p = 12 \sin 10t \quad (2)$$

The inhomogeneous term is a sine function, so the trial solution is $Q_p = A \cos 10t + B \sin 10t$.

$$Q_p = A \cos 10t + B \sin 10t \quad \rightarrow \quad \frac{dQ_p}{dt} = -10A \sin 10t + 10B \cos 10t \quad \rightarrow \quad \frac{d^2 Q_p}{dt^2} = -100A \cos 10t - 100B \sin 10t$$

Substitute these formulas into equation (2).

$$L(-100A \cos 10t - 100B \sin 10t) + R(-10A \sin 10t + 10B \cos 10t) + \frac{1}{C}(A \cos 10t + B \sin 10t) = 12 \sin 10t$$

$$\frac{A - 100ALC + 10BRC}{C} \cos 10t + \frac{B - 100BLC - 10ARC}{C} \sin 10t = 12 \sin 10t$$

Match the coefficients on both sides to get a system of equations for A and B .

$$\frac{A - 100ALC + 10BRC}{C} = 0$$

$$\frac{B - 100BLC - 10ARC}{C} = 12$$

Solving it yields

$$A = -\frac{120RC^2}{(1 - 100LC)^2 + 100R^2C^2} \quad \text{and} \quad B = \frac{12C(1 - 100LC)}{(1 - 100LC)^2 + 100R^2C^2}.$$

The particular solution is then

$$Q_p = -\frac{120RC^2}{(1-100LC)^2 + 100R^2C^2} \cos 10t + \frac{12C(1-100LC)}{(1-100LC)^2 + 100R^2C^2} \sin 10t,$$

and the general solution to the original ODE is

$$\begin{aligned} Q(t) &= Q_c + Q_p \\ &= \exp\left(-\frac{R}{2L}t\right) \left(C_3 \cos \frac{\sqrt{4LC - R^2C^2}}{2LC}t + C_4 \sin \frac{\sqrt{4LC - R^2C^2}}{2LC}t \right) \\ &\quad - \frac{120RC^2}{(1-100LC)^2 + 100R^2C^2} \cos 10t + \frac{12C(1-100LC)}{(1-100LC)^2 + 100R^2C^2} \sin 10t. \end{aligned}$$

Differentiate it with respect to t .

$$\begin{aligned} \frac{dQ}{dt} &= -\frac{R}{2L} \exp\left(-\frac{R}{2L}t\right) \left(C_3 \cos \frac{\sqrt{4LC - R^2C^2}}{2LC}t + C_4 \sin \frac{\sqrt{4LC - R^2C^2}}{2LC}t \right) \\ &\quad + \exp\left(-\frac{R}{2L}t\right) \left(-C_3 \frac{\sqrt{4LC - R^2C^2}}{2LC} \sin \frac{\sqrt{4LC - R^2C^2}}{2LC}t \right. \\ &\quad \left. + C_4 \frac{\sqrt{4LC - R^2C^2}}{2LC} \cos \frac{\sqrt{4LC - R^2C^2}}{2LC}t \right) \\ &\quad + \frac{1200RC^2}{(1-100LC)^2 + 100R^2C^2} \sin 10t + \frac{120C(1-100LC)}{(1-100LC)^2 + 100R^2C^2} \cos 10t \end{aligned}$$

Apply the initial conditions to determine C_3 and C_4 .

$$Q(0) = C_3 - \frac{120RC^2}{(1-100LC)^2 + 100R^2C^2} = 0.001$$

$$\frac{dQ}{dt}(0) = -\frac{R}{2L}C_3 + C_4 \frac{\sqrt{4LC - R^2C^2}}{2LC} + \frac{120C(1-100LC)}{(1-100LC)^2 + 100R^2C^2} = 0$$

Solving this system yields

$$C_3 = \frac{1}{1000} + \frac{120RC^2}{(1-100LC)^2 + 100R^2C^2}$$

$$C_4 = \frac{RC + 100C^2[(1200 + R)(-2L + CR^2) + 100CL^2(2400 + R)]}{1000\sqrt{4LC - R^2C^2}[(1-100LC)^2 + 100R^2C^2]}.$$

Therefore,

$$Q(t) = \exp\left(-\frac{R}{2L}t\right) \left\{ \left[\frac{1}{1000} + \frac{120RC^2}{(1-100LC)^2 + 100R^2C^2} \right] \cos \frac{\sqrt{4LC - R^2C^2}}{2LC}t \right. \\ \left. + \frac{RC + 100C^2[(1200 + R)(-2L + CR^2) + 100CL^2(2400 + R)]}{1000\sqrt{4LC - R^2C^2}[(1-100LC)^2 + 100R^2C^2]} \sin \frac{\sqrt{4LC - R^2C^2}}{2LC}t \right\} \\ - \frac{120RC^2}{(1-100LC)^2 + 100R^2C^2} \cos 10t + \frac{12C(1-100LC)}{(1-100LC)^2 + 100R^2C^2} \sin 10t.$$


Plug in $R = 24 \Omega$, $L = 2 \text{ H}$, and $C = 0.005 \text{ F}$.

$$Q(t) = e^{-6t}(0.051 \cos 8t + 0.03825 \sin 8t) - 0.05 \cos 10t$$

Differentiate this with respect to t to get the current.

$$I(t) = \frac{dQ}{dt} = -6e^{-6t}(0.051 \cos 8t + 0.03825 \sin 8t) + e^{-6t}(-0.408 \sin 8t + 0.306 \cos 8t) + 0.5 \sin 10t \\ = -0.6375e^{-6t} \sin 8t + 0.5 \sin 10t$$

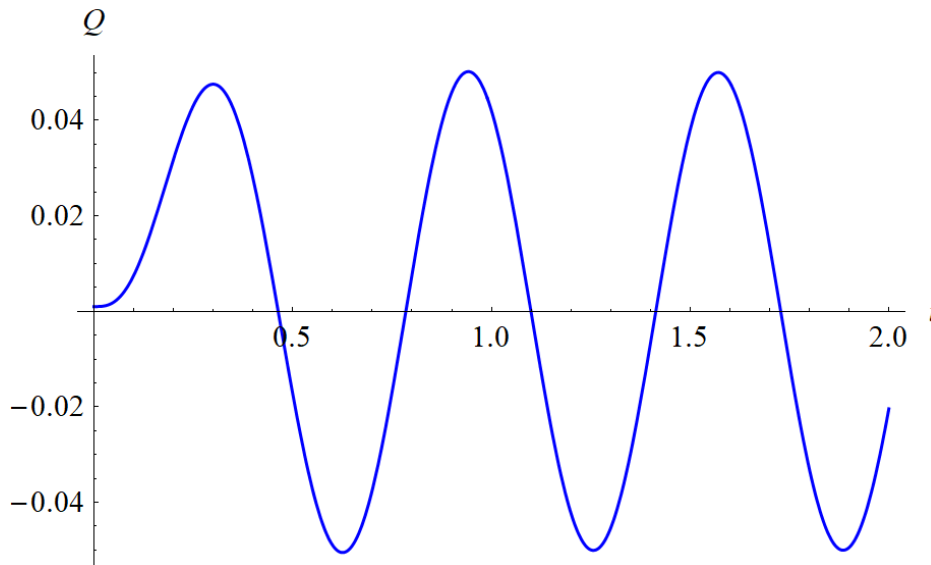Below is a plot of the charge versus time.



Below is a plot of the current versus time.

